
# An-Najah National University Faculty of Engineering and Information Technology Computer Engineering Department
 
## Digital Circuit Design II (10636321) Due to 31/07/2021

HW1: (ILOs: III) Points:20

Given the ASM chart in the attached image file for the following machine



Write a complete **VHDL** code to implement the architecture <u>using 3 processes</u>. (Use a positive edge **CLK** and a low-level asynchronous **Reset**)

,


#### You have to submit two files:

- 1. A VHDL code to implement your ASM.
- 2. A testbench file to simulate and test your design. You should cover the following two test cases in the following sequence:

#### Test Case #1:

Reset	P1	P2	Р3	C1	C2	С3	C4	Duration
0	-	-	-	-	-	-	-	2 Clock Cycles
1	0	0	0	0	0	0	0	2 Clock Cycles
1	1	0	0	0	0	0	0	2 Clock Cycles
1	0	0	0	0	0	0	0	2 Clock Cycles
1	0	0	0	1	0	0	0	1 Clock Cycle
1	0	0	0	0	0	0	0	3 Clock Cycle
1	0	0	0	0	1	0	0	1 Clock Cycle
1	0	0	0	0	0	0	0	3 Clock Cycle
1	0	0	0	0	0	1	0	1 Clock Cycle
1	0	0	0	0	0	0	0	10 Clock Cycles

 The expected result: one pulse on V1 and 2 pulses on R2




.

### Test Case #2:

Reset	P1	P2	Р3	C1	C2	C3	C4	Duration
0	1	-	-	-	-	-	-	2 Clock Cycles
1	0	0	0	0	0	0	0	2 Clock Cycles
1	0	0	1	0	0	0	0	2 Clock Cycles
1	0	0	0	0	0	0	0	2 Clock Cycles
1	0	0	0	1	0	0	0	1 Clock Cycle
1	0	0	0	0	0	0	0	3 Clock Cycle
1	0	0	0	0	0	1	0	1 Clock Cycle
1	0	0	0	0	0	0	0	3 Clock Cycle
1	0	0	0	0	0	0	1	1 Clock Cycle
1	0	0	0	0	0	0	0	10 Clock Cycles

 The expected result: one pulse on V3, 2 pulses on R2 and 1 pulse on R3



`

Note: When you select the simulation tool to be "Aldec Rivera Pro 2020.04", do not forget to set the Run Time to be sufficient to cover the previous test cases.



,